

University of California, San Diego
M.S. Exam: Computer Engineering
Fall 2014

Name: _____

Instructions:

All work to be done on the attached sheets. Write your name at the top of every sheet. 25 points/problem.

1. Consider the function $F = (AB+C+DE)'$



a. Design a transistor-level implementation of a single-stage static CMOS logic gate which minimizes the number of transistors. In your implementation, consider that input C is on the critical path, and inputs A and D are the next most important signals.

b. Show the sizes of the transistors needed to obtain the same worst-case drive as a unit inverter. (Assume P mobility is 1/2 that of N.)

c. Compute the logical effort of each of the five inputs.

d. Assuming all diffusion is fully contacted, estimate the Elmore delay when A, C, and D all fall from 1 to 0, while B and E remain at 1.

2. Consider the following two circuits:

  

2a) What are the logic functions implemented here?

2b) What is the probability of switching at each node given that $P_A = P_C = P_D = 1/2$, and $P_B = 1/4$?

2c) Which circuit features the lowest power consumption? Quantify your result. You can neglect the switching power of the inputs.

M. S. Exam: Computer Engineering

3. Using NAND, NOR, and XOR gates, design a **comparator** which performs the following function:

```
if (A - B = k) output = 1;  
else          output = 0;
```

where inputs A, B, and k are 4-bit two's complement numbers and the output is a single bit. You may sketch the gates, write Verilog code, etc.

4. Consider a state machine comprising a flip-flop and a combinational circuit wired in a loop, i.e., the output of the flip-flop drives the combinational circuit, and the output of the combinational circuit drives the data input of the flip-flop.

For $f_{\text{clock}} = 2\text{GHz}$, and flip-flop parameters of:

$t_{\text{setup}} = 65\text{ps}$, $t_{\text{hold}} = 30\text{ps}$, $t_{\text{clk-toQ}} = 50\text{ps}$, and $t_{\text{contamination_dly}} = 35\text{ps}$, compute:

4a) the maximum allowable $t_{\text{propagation_delay}}$ for the combinational logic (0 clock jitter);

4b) repeat 4a) for jitter of up to $\pm 50\text{ps}$ from one clock rising edge to the next

4c) the minimum allowable $t_{\text{contamination_delay}}$ for the combinational logic (no jitter);

4d) repeat 4c) for $\pm 50\text{ps}$ jitter