

University of California, San Diego

M.S. Exam: Logic Design (CSE140)

Spring 2014

NAME : _____

Question 1. [20 pts]

(a) [10 pts] Using Boolean algebra theorems, simplify F to a minimum sum-of-products.

- Your answer should have five terms exactly.
- Write all steps to answer. Do not write the name of Boolean algebra theorem.

$$F = (A + B' + C + E') \cdot (A + B' + D' + E) \cdot (B' + C' + D' + E')$$

(b) [10 pts] Find the minterm expansion of f .


$$f(a, b, c, d) = a'b' + a'd + acd'$$

$$f = \sum m(\quad)$$

Question 2. [20 pts]

$$F(a, b, c, d, e) = \sum m(0, 3, 4, 5, 6, 7, 8, 12, 13, 14, 16, 21, 23, 24, 29, 31)$$

(a) [10 pts] Draw a Karnaugh map for F .

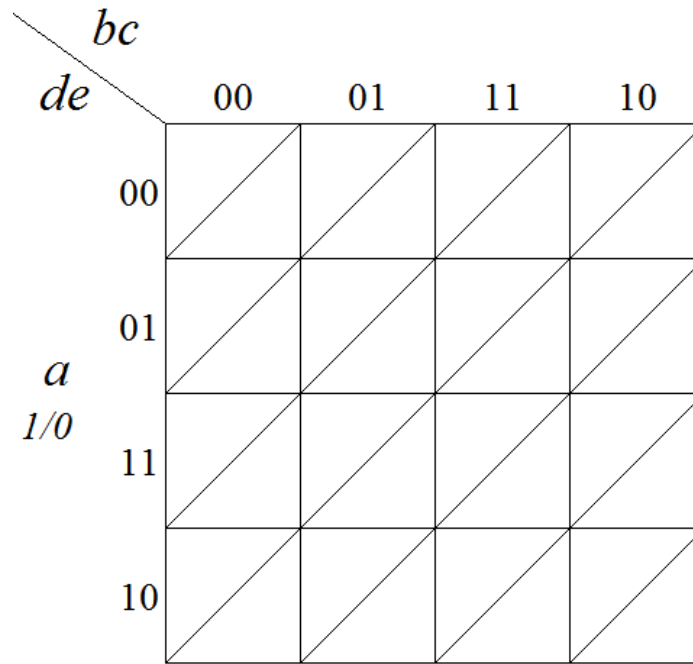

(b) [5 pts] Find the essential prime implicants (there are four essential prime implicants).

(c) [5 pts] Find all of the prime implicants (there are nine prime implicants).

Question 3. [20 pts]

- (a) **[10 pts]** Implement F with three-level NAND gate circuit. Note that you have only two (2) two-input NAND gates and two (2) three-input NAND gates available for your implementation.

$$F(A, B, C, D) = \sum m(5, 10, 11, 12, 13)$$

- (b) **[10 pts]** Implement F using one 4:1 MUX and one 2:1 MUX only. The output F should be the output of the 2:1 MUX. ($d = \text{don't care}$)


$$F(A, B, C, D) = \sum m(1, 3, 4, 5, 7, 9, 11, 14) + \sum d(8, 15)$$

Question 4. [10 pts]

(a) [5 pts] Fill the following truth table for J-K flip-flop.

| J | K | Q | Q_+ |
|-----|-----|-----|-------|
| 0 | 0 | 0 | |
| 0 | 0 | 1 | |
| 0 | 1 | 0 | |
| 0 | 1 | 1 | |
| 1 | 0 | 0 | |
| 1 | 0 | 1 | |
| 1 | 1 | 0 | |
| 1 | 1 | 1 | |

(b) [5 pts] Complete the following timing diagram for the J-K flip-flop.

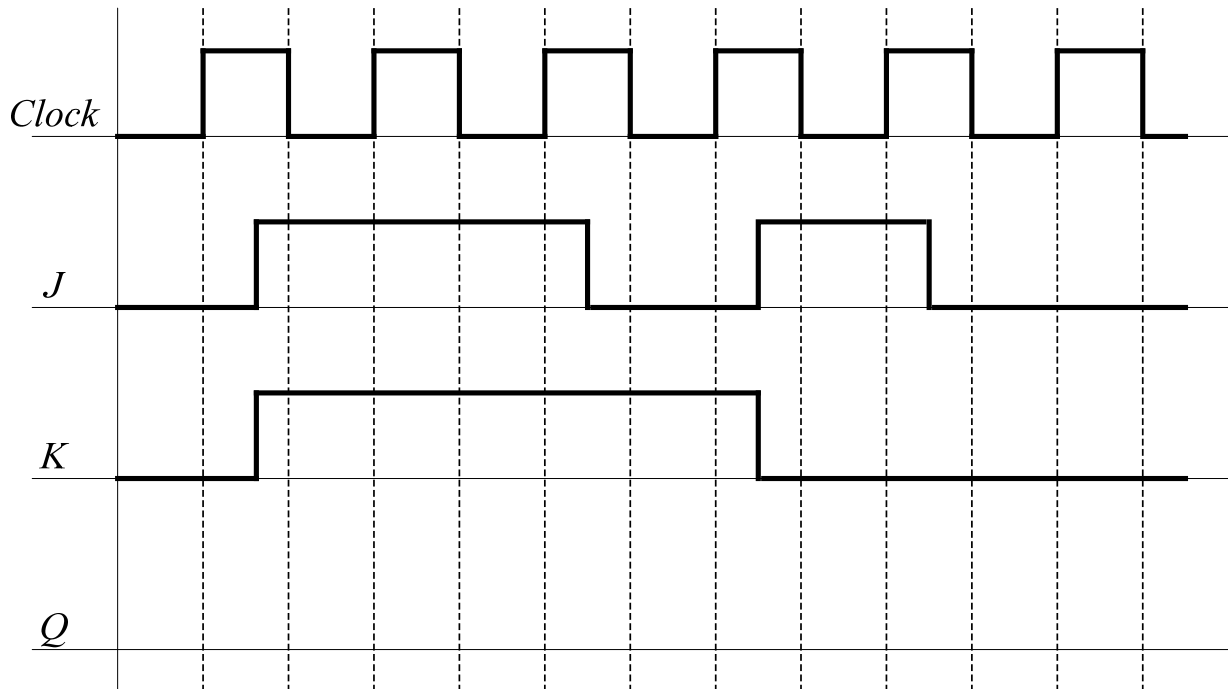

Question 5. [30 pts]

Design a 3-bit counter which counts 001, 011, 010, 110, 111, 101, 100, (repeat) 001, 011, Assume that the outputs of the flip-flops used in the counter are called (C, B, A).

(a) [10 pts] Fill the state transition table.

| C | B | A | $C+$ | $B+$ | $A+$ | J_C | K_C | J_B | K_B | J_A | K_A |
|-----|-----|-----|------|------|------|-------|-------|-------|-------|-------|-------|
| 0 | 0 | 0 | | | | | | | | | |
| 0 | 0 | 1 | | | | | | | | | |
| 0 | 1 | 0 | | | | | | | | | |
| 0 | 1 | 1 | | | | | | | | | |
| 1 | 0 | 0 | | | | | | | | | |
| 1 | 0 | 1 | | | | | | | | | |
| 1 | 1 | 0 | | | | | | | | | |
| 1 | 1 | 1 | | | | | | | | | |

(b) [10 pts] Implement the counter using D flip-flops in your circuit (sum-of-products form).

| $BA \backslash C$ | 0 | 1 |
|-------------------|---|---|
| 00 | | |
| 01 | | |
| 11 | | |
| 10 | | |

D_C

| $BA \backslash C$ | 0 | 1 |
|-------------------|---|---|
| 00 | | |
| 01 | | |
| 11 | | |
| 10 | | |

D_B

| $BA \backslash C$ | 0 | 1 |
|-------------------|---|---|
| 00 | | |
| 01 | | |
| 11 | | |
| 10 | | |

D_A

$D_C =$ _____

$D_B =$ _____

$D_A =$ _____

(c) [10 pts] Implement the counter using J-K flip-flops in your circuit. (sum-of-products form)

| | | | | | |
|-------|----|------|--|---|---|
| | | C | | | |
| | | BA | | 0 | 1 |
| J_C | 00 | | | | |
| | 01 | | | | |
| | 11 | | | | |
| | 10 | | | | |

| | | | | | |
|-------|----|------|--|---|---|
| | | C | | | |
| | | BA | | 0 | 1 |
| J_B | 00 | | | | |
| | 01 | | | | |
| | 11 | | | | |
| | 10 | | | | |

| | | | | | |
|-------|----|------|--|---|---|
| | | C | | | |
| | | BA | | 0 | 1 |
| J_A | 00 | | | | |
| | 01 | | | | |
| | 11 | | | | |
| | 10 | | | | |

| | | | | | |
|-------|----|------|--|---|---|
| | | C | | | |
| | | BA | | 0 | 1 |
| K_C | 00 | | | | |
| | 01 | | | | |
| | 11 | | | | |
| | 10 | | | | |

| | | | | | |
|-------|----|------|--|---|---|
| | | C | | | |
| | | BA | | 0 | 1 |
| K_B | 00 | | | | |
| | 01 | | | | |
| | 11 | | | | |
| | 10 | | | | |

| | | | | | |
|-------|----|------|--|---|---|
| | | C | | | |
| | | BA | | 0 | 1 |
| K_A | 00 | | | | |
| | 01 | | | | |
| | 11 | | | | |
| | 10 | | | | |

$J_C =$ _____

$J_C =$ _____

$J_B =$ _____

$J_B =$ _____

$J_A =$ _____

$J_A =$ _____