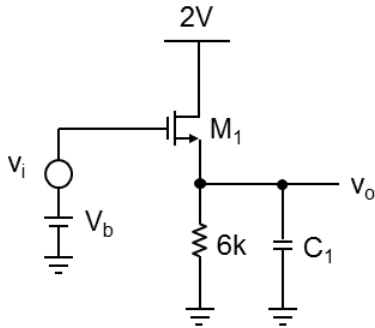


**Electronic Circuits & Systems (ECE102) - ECE MS Comp Exam, Fall 2013**


**Problem #1:**



Answer with the following parameters:  $\mu C_{ox} = 200\mu\text{A}/\text{V}^2$ ,  $V_{th} = 0.4\text{V}$ ,  $C_{ox} = 40\text{fF}/\mu^2$ , and  $W/L = 80\mu/0.2\mu$ .

1. Set the input DC bias  $V_b$  so that the output DC can be  $0.6\text{V}$ ?
2. In this bias condition, estimate the low-frequency small-signal gain  $v_o/v_i$ .
3. Calculate the pole and zero frequencies if  $C_1$  is the same as  $C_{gs}$ .
4. What is the maximum peak-to-peak output swing you can get?
5. Now if  $C_1$  is  $1\text{pF}$ , sketch the Bode gain and phase plots.

**Problem #2:**

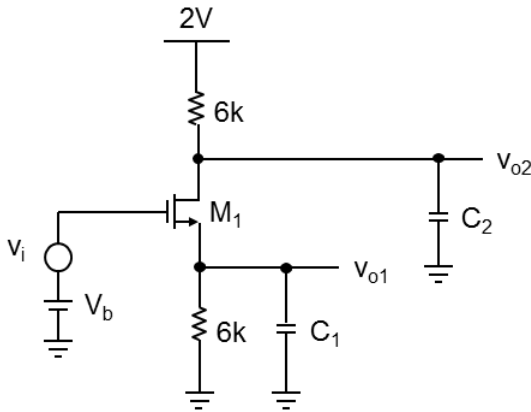

Now add a  $6\text{k}$  resistor to the drain of the same amplifier given in #1. Assume the same bias condition stays the same.

1. What is the DC voltage at the drain?
2. Explain why the low-frequency small-signal gain  $v_{o1}/v_i$  is the same as derived in #1.
3. Estimate the low-frequency small-signal gain  $v_{o2}/v_i$ .
4. If  $C_1=0$  and  $C_2=1\text{pF}$ , what is the  $-3\text{dB}$  bandwidth of this gain?
5. If  $C_1=C_2=1\text{pF}$ , explain what happens.