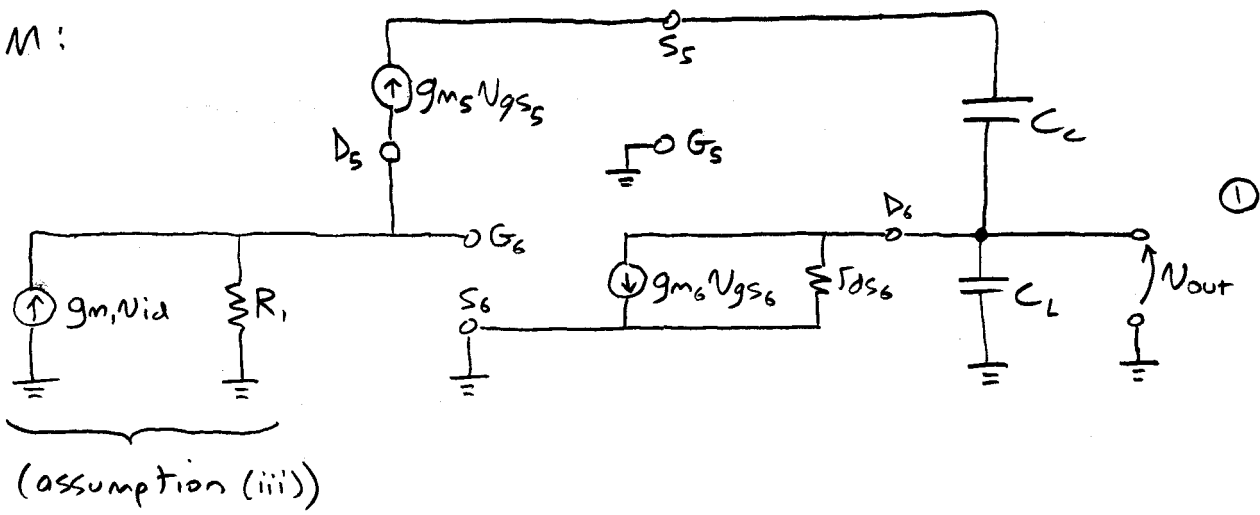


SSM:



1. Use ZVTC Theorem:

Let  $C_1 = C_c$ ,  $C_2 = C_L$  (Let  $R_1'$  and  $R_2'$  be the corresp. driving pt. resistances)  
 Inspection of ①  $\Rightarrow R_2' = r_{ds6}$

To find  $R_1'$ , set  $N_{id} = 0$ ,  $C_c = 0$ , and  $C_L = 0$ , and insert a test source  $N_x$  across  $S_5$  and  $D_6$ . Then  $R_1' = N_x / i_x$  where  $i_x =$  current through the test source:

$$\left. \begin{aligned} V_{out} &= -r_{ds6} (i_x + g_{m6} N_{gs6}) \\ V_{gs6} &= i_x R_1 \end{aligned} \right\} \Rightarrow \underbrace{V_{out} = -i_x r_{ds6} (1 + g_{m6} R_1)}_{\textcircled{2}}$$

$$\left. \begin{aligned} V_{out} + N_x + V_{gs5} &= 0 \\ g_{m5} V_{gs5} &= -i_x \end{aligned} \right\} \Rightarrow \underbrace{V_{out} = -N_x + i_x / g_{m5}}_{\textcircled{3}}$$

$$\textcircled{2}, \textcircled{3} \Rightarrow -i_x r_{ds6} (1 + g_{m6} R_1) - i_x / g_{m5} = -N_x$$

$$\therefore R_1' = r_{ds6} (1 + g_{m6} R_1) + 1/g_{m5}$$

$$\therefore \boxed{\omega_{-3dB} \approx \frac{1}{C_c [r_{ds6} (1 + g_{m6} R_1) + 1/g_{m5}] + C_L r_{ds6}}} \quad \textcircled{4}$$

2. KCL at  $G_6$

$$\frac{V_{gs6}}{R_1} - g_{m1}V_{id} + g_{m5}(0 - V_{s5}) = 0$$

$$\therefore V_{gs6} = R_1 (g_{m1}V_{id} + g_{m5}V_{s5}) \quad (5)$$

KCL at  $S_5$

$$-g_{m5}(0 - V_{s5}) + (-V_{s5} - N_{out}) \cdot sC_c = 0$$

$$V_{s5} (g_{m5} + sC_c) = N_{out} \cdot sC_c$$

$$\therefore V_{s5} = N_{out} \cdot \frac{sC_c}{g_{m5} + sC_c} \quad (6)$$


KCL at  $D_6$

$$g_{m6}V_{gs6} + \frac{N_{out}}{r_{ds6}} + N_{out} \cdot sC_c + (N_{out} - (V_{s5}))sC_c = 0$$

$$N_{out} \left[ \frac{1}{r_{ds6}} + s(C_c + C_c) \right] = -g_{m6}V_{gs6} + sC_c V_{s5}$$

$$N_{out} = \frac{-g_{m6}r_{ds6}V_{gs6} + sC_c r_{ds6}V_{s5}}{1 + s(C_c + C_c) \cdot r_{ds6}} \quad (7)$$

(5) - (7)  $\Rightarrow$  B.D. :

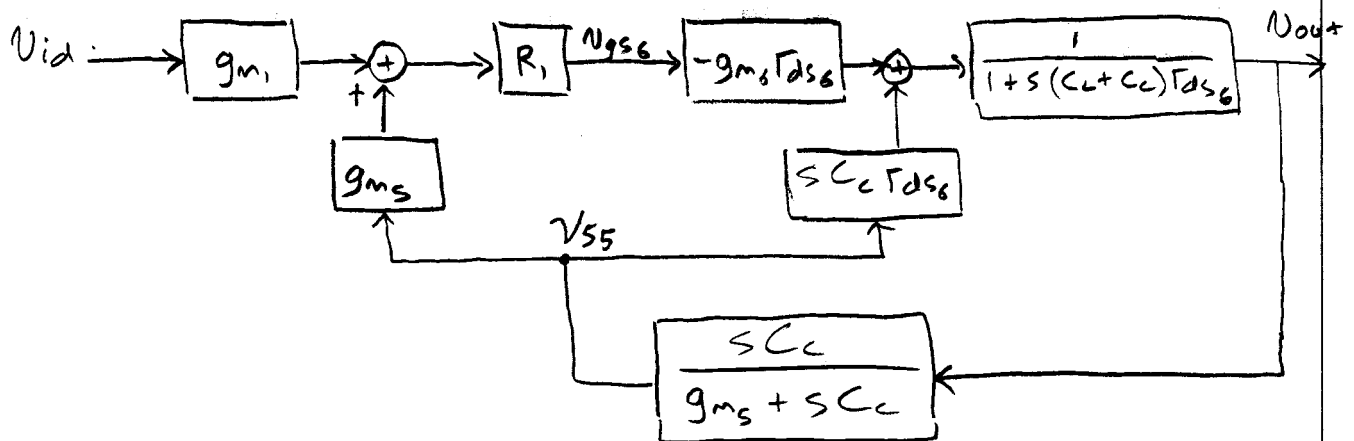

3.

$$P_1 = \underbrace{-g_{m1} R_1 g_{m6} \Gamma_{ds6}}_{\text{call } a_0} \frac{1}{1 + s(C_L + C_c) \Gamma_{ds6}}$$

$$L_1 = -g_{m5} R_1 g_{m6} \Gamma_{ds6} \frac{s C_c}{(1 + s(C_L + C_c) \Gamma_{ds6})(g_{m5} + s C_c)}$$

$$L_2 = \Gamma_{ds6} \frac{s^2 C_c^2}{(1 + s(C_L + C_c) \Gamma_{ds6})(g_{m5} + s C_c)}$$

$$1 - L_1 - L_2 = \frac{(1 + s(C_L + C_c) \Gamma_{ds6})(g_{m5} + s C_c) + a_0 \left(\frac{g_{m5}}{g_{m1}}\right) s C_c - \Gamma_{ds6} s^2 C_c^2}{(1 + s(C_L + C_c) \Gamma_{ds6})(g_{m5} + s C_c)}$$

$$\therefore a(s) = \frac{P_1}{1 - L_1 - L_2}$$

$$a(s) = a_0 \frac{g_{m5} + s C_c}{(1 + s(C_L + C_c) \Gamma_{ds6})(g_{m5} + s C_c) + a_0 \left(\frac{g_{m5}}{g_{m1}}\right) s C_c - \Gamma_{ds6} s^2 C_c^2}$$

$$a(s) = a_0 \frac{g_{m5} + s C_c}{g_{m5} + s \left[ (C_L + C_c) \Gamma_{ds6} g_{m5} + a_0 \left(\frac{g_{m5}}{g_{m1}}\right) C_c + \frac{C_c^2}{g_{m5}} \right] + s^2 C_L C_c \Gamma_{ds6}}$$

$$a(s) = a_0 \frac{1 + s C_c / g_{m5}}{1 + s \underbrace{\left[ (C_L + C_c) \Gamma_{ds6} + R_1 g_{m6} \Gamma_{ds6} \frac{C_c + C_c / g_{m5}}{g_{m5}} \right]}_{\text{call } \beta} + s^2 C_L C_c \Gamma_{ds6} / g_{m5}} \quad (5)$$

Note: (4) =  $1/\beta \Rightarrow$  consistent with prob. 1.

4. denom of (5) =  $1 + \beta s + \alpha s^2$

$$\therefore \boxed{P_1 = -\frac{1}{\beta} \approx -\frac{1}{R_1 g_{m6} \Gamma_{ds6} C_c}}$$

$$\boxed{P_2 = -\beta/\alpha \approx -\frac{R_1 g_{m6} g_{m5}}{C_L}}$$

$$\boxed{z = -\frac{g_{m5}}{C_c}}$$