

Spring 2015 M.S. Comprehensive Exam

Electronic Circuits and Systems (ECE 166/265)

Problem 1:

a) Design an *LC matching network* which matches a load of $Z_L = 30 - j150 \Omega$ to a generator impedance of $60 + j40 \Omega$. Do not design two independent matching networks with each one to 50Ω . Use the Smith Chart.

b) Consider the following 4-port network with general S-parameters and $S_{22} = S_{44} = 0$ and $S_{23} = S_{43} = 0$. Calculate S_{11} of the network when connected as follows. Use the S-parameter matrix or follow the waves (all of them). Note that S_{42} and S_{24} are not equal to zero.

