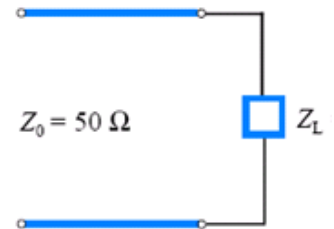



# Electricity & Magnetism (ECE 107) – ECE MS Comp Exam, Fall 2013

A 50-Ω lossless line is terminated with a load impedance  $Z_L = (50+j50) \Omega$ .  
 (a) Calculate  $\Gamma$  and S.



(b) find a value for  $l_{max}$  where there is the first voltage maximum assuming a wavelength  $\lambda$  of the signal.

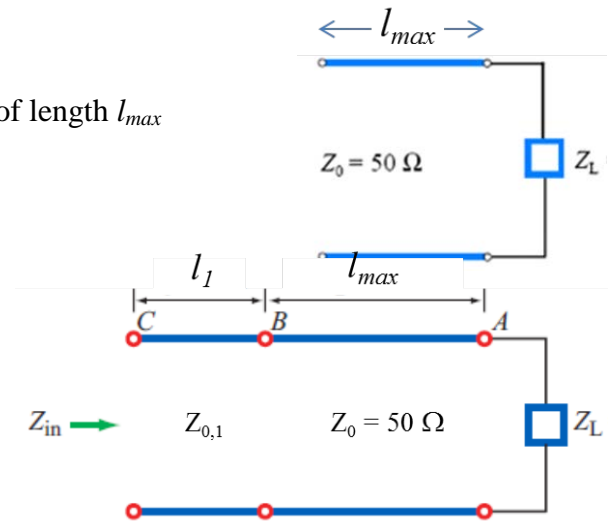(c) Calculate the input impedance for the transmission line of length  $l_{max}$



(d) Now add a second transmission line of length  $l_1$  and impedance  $Z_{0,1}$ . Choose values for  $l_1$  (in terms of  $\lambda$ ) and impedance  $Z_{0,1}$  so that the input impedance at point C would match a 50-Ω transmission line.

(e) Assuming that the two transmission lines shown in (d) are connected to a 50-Ω transmission line that is connected to a signal generator ( $Z_g = 50 \Omega$  and  $V_g = 10 \text{ V}$ ), how much power is being delivered to the load?